


CSE205 Spring 2021 Homework 4

John J Li

March 18, 2021

 Problem 1


Compute the maximum delay, assume every gate (gate includes the attached negation bubbles) has a delay of Δ . Assume only uncomplemented inputs are available and an additional gate must be added to complement any input marked X'.



Solution: Since we can see that inputs A and E will have to go through 6 logic gates and we assumed every gate has a delay of Δ , the maximum delay is 6Δ .

 Problem 2

Create the truth table that belongs to the following multiplexer implementing function $F(A, B, C)$.



Solution:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Problem 3

Given the following functions,


$$F(A, B, C) = \sum m(1, 4, 5, 7)$$

$$G(A, B, C) = \prod M(1, 2, 3, 4, 7)$$

a. Implement both functions using a PROM chip (draw full grid)


Solution:

A	B	C	F	A	B	C	G
0	0	0	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	0
1	0	0	1	1	0	0	0
1	0	1	1	1	0	1	1
1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	0

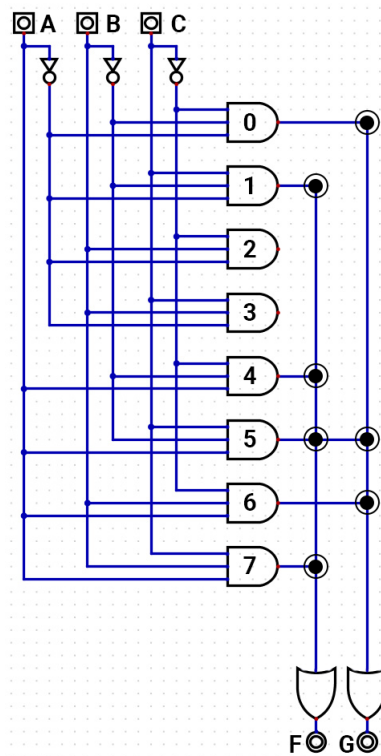

b. Implement both function using as many 2:4 decoders chips (with a single active lowenable) and any other logic gates needed

Solution:

 


Problem 4

We have a new type of flip flop with inputs A and B. If $A = 0$, then $Q^+ = B' + Q$. If $A = 1$, then $Q^+ = (AB)'$.

a. Show the state diagram for this flip flop.

Solution:

A	Q	Q ⁺	B
0	0	0	1
	0	1	0
	1	0	0
	1	1	1
1	0	0	0
	0	1	1
	1	0	0
	1	1	1

 

b. Write a single equation for Q^+ in terms of A, B and Q.

Solution:

A	BQ			
	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$$Q^+ = Q(A+B) + A'B'Q'$$

Problem 5

Answer the following short answer questions:

a. Why is a NOT inverter logic gate faster than an open-collector buffer gate?

Solution: An open-collector buffer gate consists of two transistors. This, by default, would mean that the NOT inverter logic gate is faster than an open-collector buffer gate since a NOT inverter gate only contains one transistor.

b. What happens when a tri-state buffer has an enable input equal to 0?


Solution: When the tri-state buffer has an enable input equal to 0, the buffer behaves as an open circuit – the output is no longer connect to anything. This is called the High-Impedance state (Hi-Z).

c. A latch and a flip flop differ in what way?


Solution: Latches are asynchronous – the outputs changes soon after the input changes – however, most appliances and electronics operate with an internal clock signal. And so the flip-flop is a synchronout version of the latch meaning it incorporates a clock signal so that the outputs changes simultaneously according to the clock.

 Problem 6

For the input D show below, show the D-latch output (Q) assuming the latch is activated when the enable signal is high.



Solution:

 


Problem 7

Create the schematic for a new flip flop with the behavior defined by the function below. Use a single D flip flop (positive edge triggered), a single 2:1 multiplexer, and any complemented or uncomplemented variables or additional logic gates needed.

$$Q^+(x, y, Q) = (Q' + x) + (y'Q')$$


Solution:

x	y	Q	Q ⁺
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

 
Problem 8

For the input shown below, show the flip flop outputs assuming a negative edge trigger.




- a. Assume that the flip flop is a T flip flop with only an active low clear (ignore the PRE' input).

Solution:

 



- b. Assume that the flip flop is a D flip flop with both an active low clear and active low preset.

Solution:

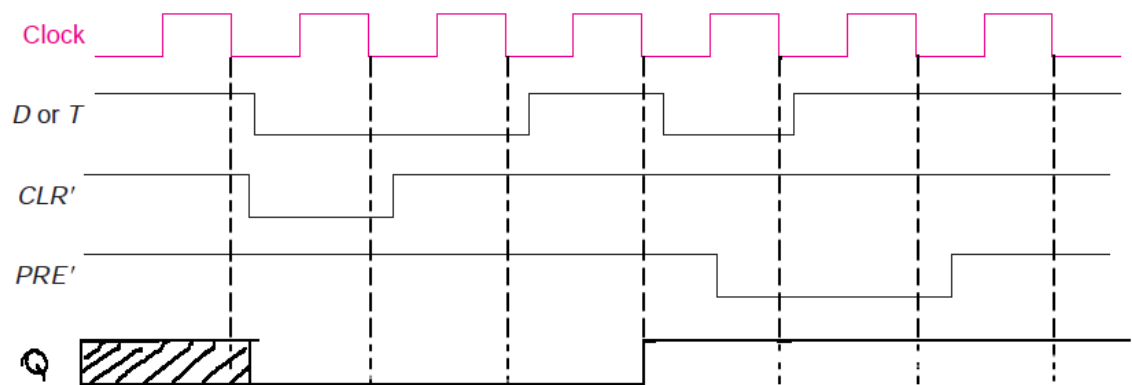

  
Problem 9


For the following JK flip flop, complete each timing diagram. First, assume the CLR' and PRE' are inactive (1). Then use the values shown.





Solution:

J	K	Q^+
0	0	Q
0	1	0
1	0	1
1	1	\overline{Q}

 


 

Solution:

 
 


Solution:

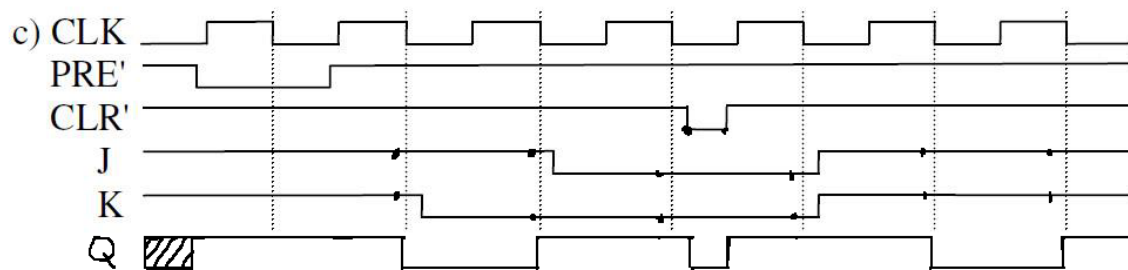

  
Problem 10

For the following circuit, complete the timing diagram assuming negative edge triggering. Include a timing graph for both IN and Q in relation to x. Assume the flip flop is a D flip flop. Assume the flip flop starts at 0.




Solution:

IN equation: $\overline{Q}x + Q\overline{x}$

 


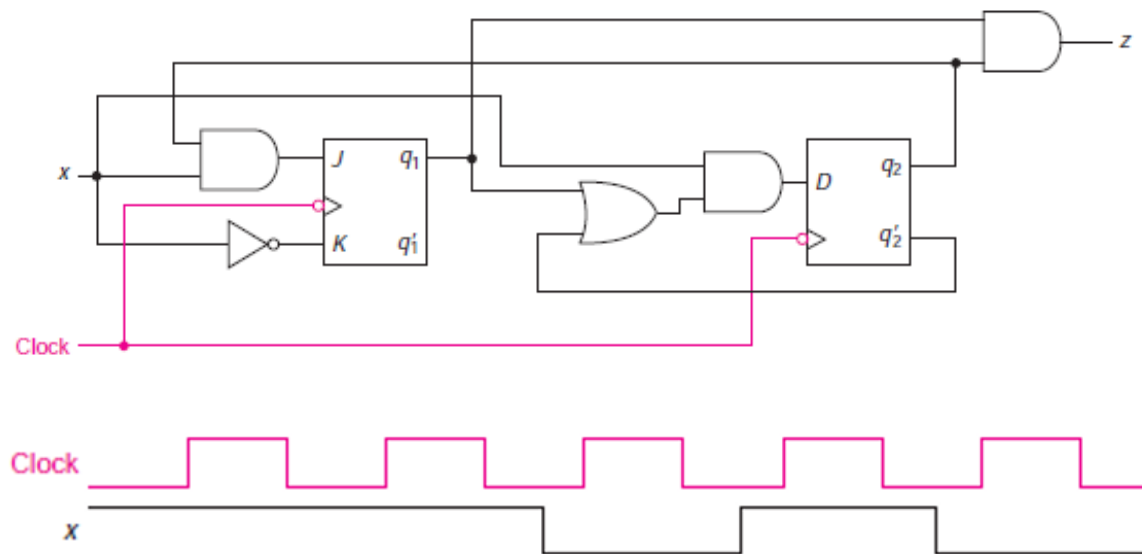Problem 11

For the following circuit, complete the timing diagram for the state of each flip flop and the output, where shown. All flip flops are negative-edge triggered. Assume each flip flop starts at 0.



Solution:

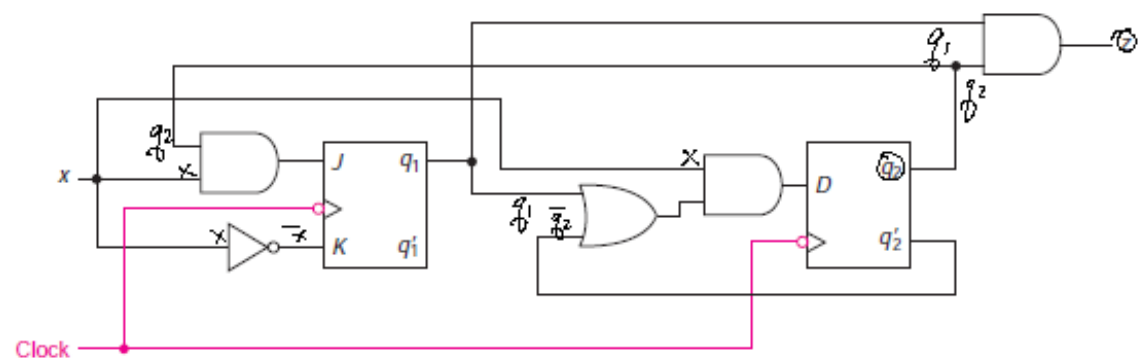

$$J = xq_2 \quad K = \bar{x} \quad D = x(q_1 + \bar{q}_2) \quad Z = q_1q_2$$

